

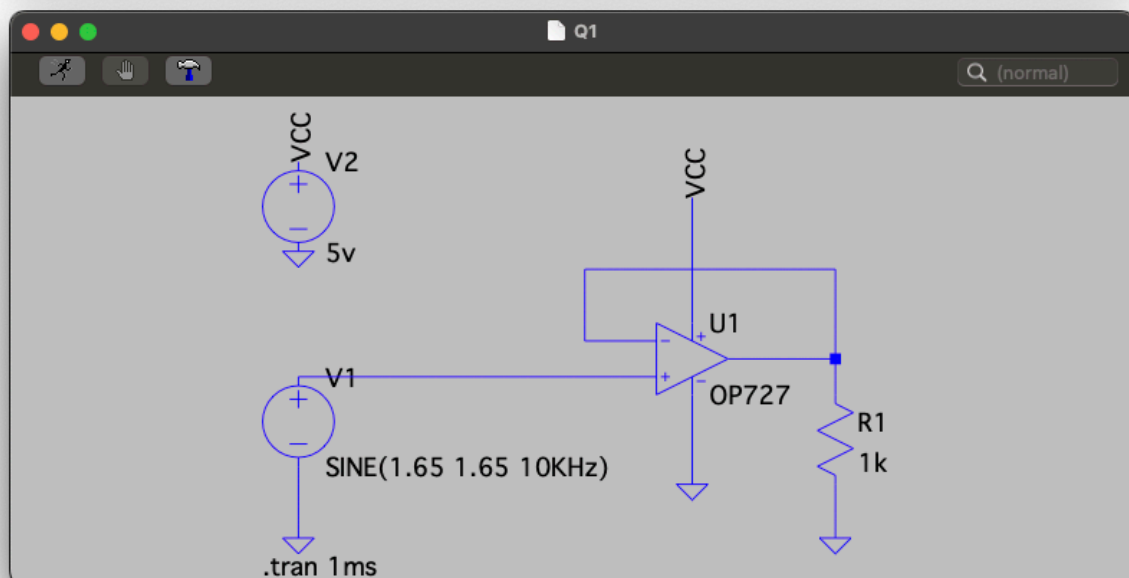
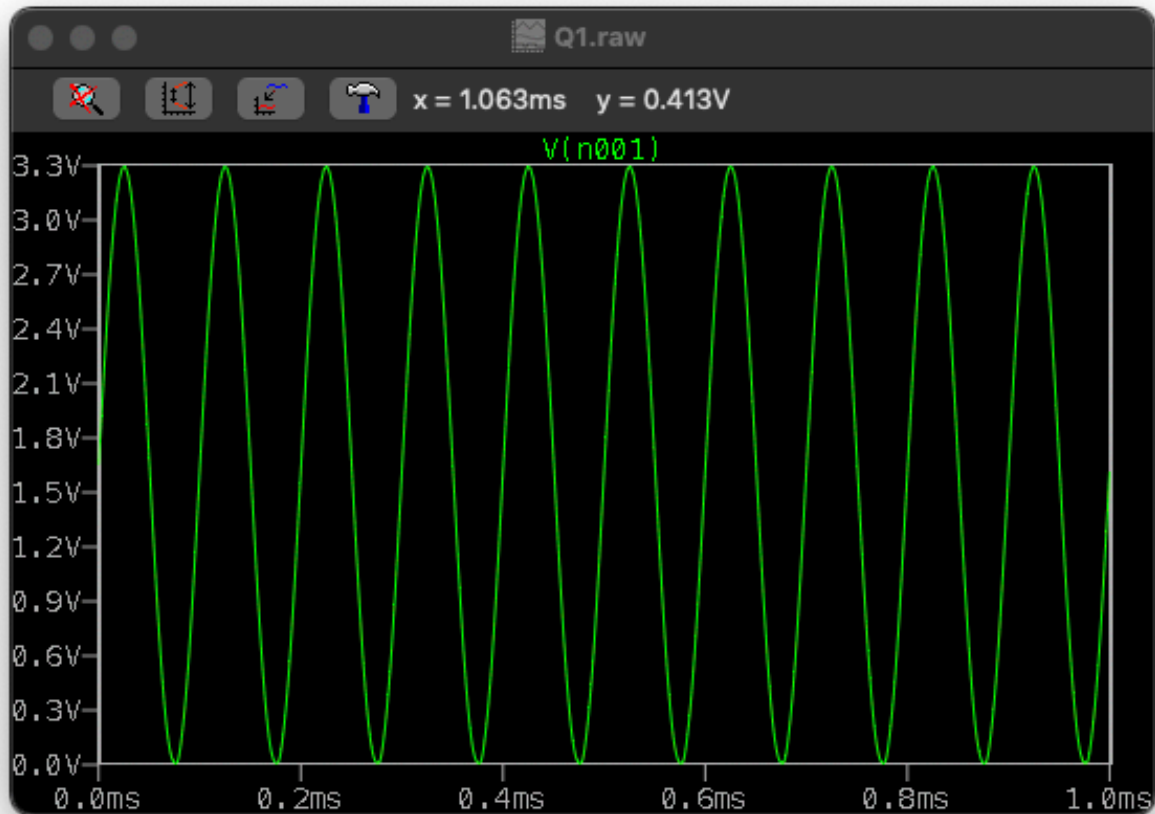


Embedded Sys Lab: Op-amp Assignment



1. Voltage Follower

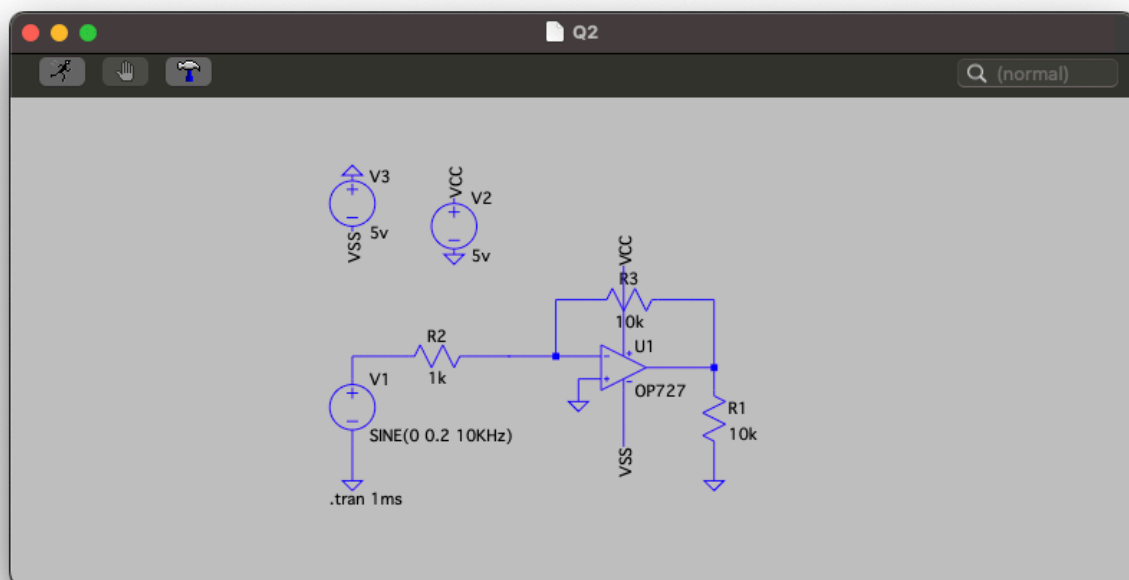

2. Inverting Amplifier

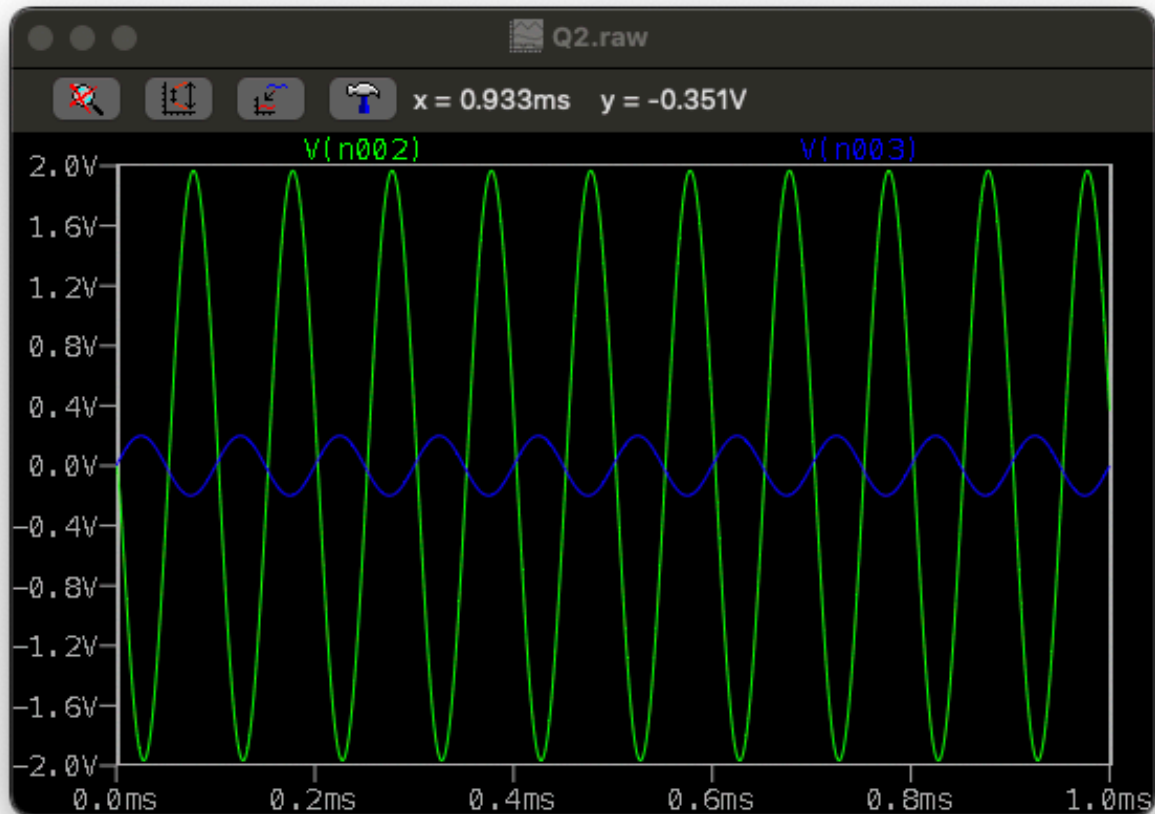

3. Non-inverting amplifier

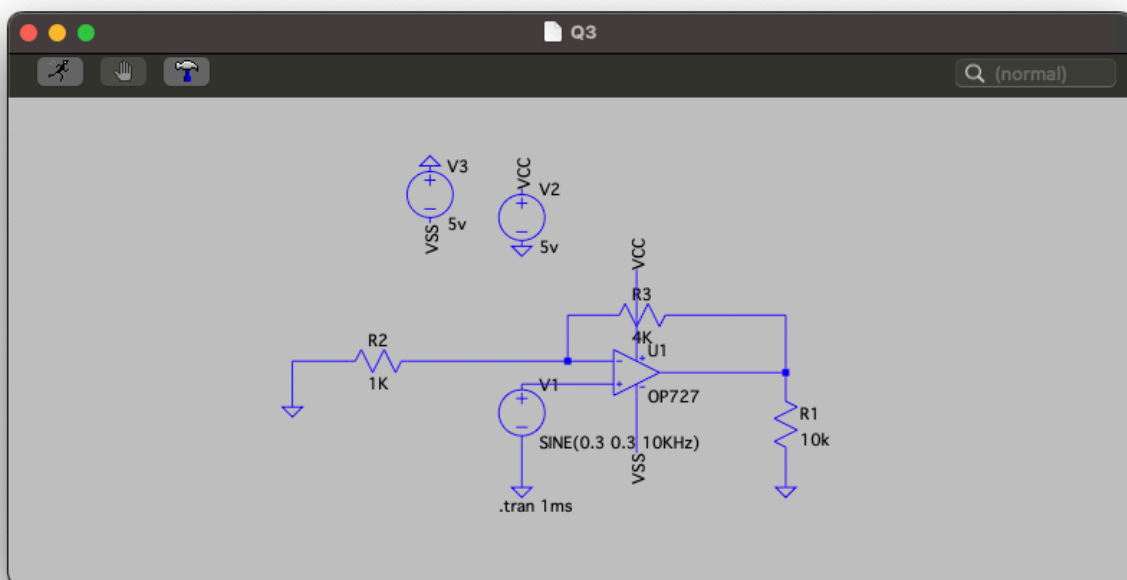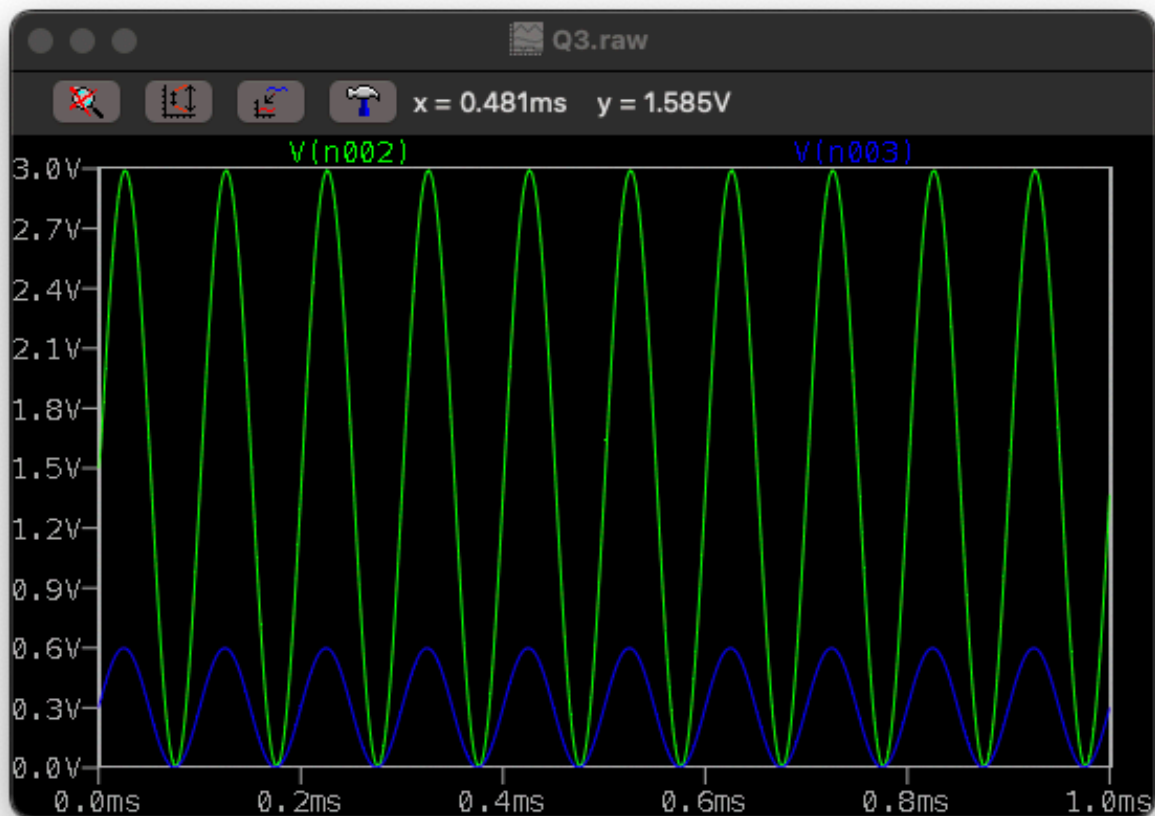

4. Current Source

